
Programmable Digital Display

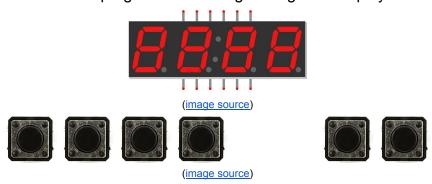A user-programmable 4-digit 7-segment display




How it works

- ·Each digit (all four) has a corresponding button allowing user to iterate through numbers (1-9) and alphabet (A-F)
- ·The "Program/Erase" button allows the user to either save the current set of characters, or erase it along with all other stored sets.
 - ->To save, the user will press the button once. Display will then be reset and wait for next inputs.
 - ->To erase, the user will press the button twice. Display will then be reset and wait for new inputs.
- ·The "Play/Stop" button either begins playing the programmed character sets, or stops the ones that are currently playing.

Schematic

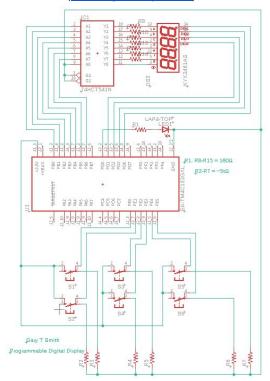(<u>KYX-3561AS display library source</u> - custom converted to KYX-3461AS) (<u>tm4c123gxl library source</u>)



Part List

1x <u>Tiva C Launchpad</u> dev board w/ <u>TM4C123GH6P</u> mcu 1x <u>KYX-3461AS</u> four-digit 7seg display 1x 5mm <u>Red LED</u> 4x Pushbutton

Calculations/Notes

V=IR

 R_{seq} = 3.3 V/0.01 A = $\sim \! 330 \Omega$ = 180Ω or 183Ω actual (Feed 10mA to each segment LED, max 25mA)

 $R_{\text{button_pulldown}}\text{=}\text{\sim}10k\Omega~\text{\tiny (General rule-of-thumb)}$

 R_{red} =3.3V/0.01A=~330 Ω (Feed 10mA to red LED, max 20mA)

Connected DP to GND instead of Y8 like schematic. A8 unconnected.

Will utilize multiplexing to display all 4 digits, with 5ms delay between each.

Decided to not implement "erase" functionality in initial build. Use TIVA reset button.

Issues/Changelog

Change LED pin from P7 to 0 due to lock on PD7[3/1/21] Pins not supplying full 3.3V, must figure out why [3/1/21]

Attempting to mitigate voltage drop from possible *loading effect* by adding buffer opamp to circuit[3/2/21]

Determined issue to be excessive GPIO power draw, ordered buffer IC chip [3/2/21]

Installed buffer chip 74HC541N, problem resolved. Updated schematic! [3/4/21]

Problem with code simulator, switched to a pre-made template [3/6/21]

Changed buttons from port A to port E due to lock[3/6/21]
Updated schematic [3/6/21]